

### Homework #4

Due Thursday, May 25, 2017, at 2:30 PM


*Collaboration and discussions are not allowed on Problem 1  
 and are allowed and encouraged on Problem 2*

This homework set is based on *C. E. Shannon's Masters Thesis from 1938, "A Symbolic Analysis of Relay and Switching Circuits"*. This classical paper was the first work that connected between logic and circuit design. We encourage you to read this thesis, it is posted on the class web site.

**Please note** that Shannon used the dual notation, however, in this homework set we expect you to use the notation from class, namely, 0 corresponds to an open relay and 1 to a closed relay.

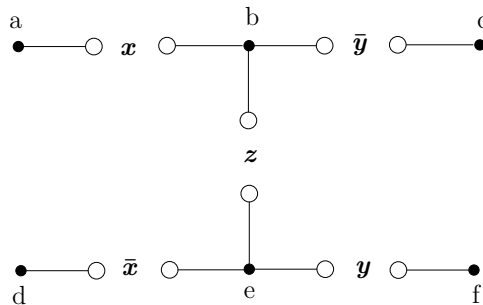1. **A Generalization to Multiple Terminals** (*Collaboration is not allowed on this Problem*)

A generalization of the switching (relay) circuit model is a circuit with multiple terminals. The Boolean function  $X_{ab}$  is 1 if there is a closed path between terminals  $a$  and  $b$ , and 0 otherwise. With multiple terminals,  $a, b, c, d, \dots$ , Boolean functions exist between any *pair* of terminals. For example, for the circuit



we have

$$\begin{aligned} X_{af} &= x \cdot y \cdot z \\ X_{bd} &= \bar{x} \cdot z \\ X_{cf} &= 0 \end{aligned}$$

and so on.

- (a) Construct a circuit with 3 relays that implements the functions

$$f_1 = x \cdot y$$

$$f_2 = \bar{x} \cdot y$$

- (b) Construct a circuit with 4 relays that implements the functions

$$f_1 = x \cdot y + \bar{x} \cdot \bar{y}$$

$$f_2 = \bar{x} \cdot y + x \cdot \bar{y}$$

- (c) Construct a circuit with 6 relays that implements the functions:

$$f_1 = x \cdot (y + z)$$

$$f_2 = y \cdot (x + z)$$

$$f_3 = z \cdot (x + y)$$

$$f_4 = x + y \cdot z$$

$$f_5 = y + x \cdot z$$

$$f_6 = z + x \cdot y$$

- (d) *Extra Credit: 10% of the total homework grade.* Construct a circuit with as few relays as possible that implements all 16 functions of two variables. A solution with 8 relays gets full credit.

2. **The Complete Quadratic Function** (*Collaboration is allowed on this Problem*)

The Complete Quadratic (CQ) function is the Boolean function that consists of the XOR of all the  $\binom{n}{2}$  possible AND's between pairs of inputs. Namely,

$$CQ(X) = (x_1 \cdot x_2) \oplus (x_1 \cdot x_3) \oplus \cdots \oplus (x_{n-1} \cdot x_n).$$

For example,

$$CQ(x_1, x_2, x_3) = (x_1 \cdot x_2) \oplus (x_1 \cdot x_3) \oplus (x_2 \cdot x_3).$$

- (a) In class we proved that a Boolean function  $f(X)$  is symmetric iff it is a function of  $|X|$  (the number of 1s in  $X$ ). Write  $CQ(X)$  with 6 inputs as a function of  $|X|$ . Note that there are 7 entries in the table.
- (b) Generalization: For an arbitrary  $n$ , express  $CQ(X)$  as a function of  $|X|$ . Namely, you need to specify, as a mathematical expression, the values of  $|X|$  for which  $CQ(X) = 1$ . Justify your solution.
- (c) Construct a circuit for  $CQ(X)$  with five inputs, namely,  $X \in \{0, 1\}^5$ . Please use as few relays as possible. A solution with 20 relays (or less) gets full credit. Justify your solution.

*Hint:* Use the construction of XOR from class as an inspiration.