

Homework #5


Due Tuesday, June 6, 2017, at 2:30 PM

*Collaboration and discussions are not allowed on Problem 1
and are allowed and encouraged on Problem 2*


1. **Stochastic Switching Circuits** (*Collaboration is not allowed on this Problem*)

In this problem we study the synthesis and analysis of stochastic switching circuits. In particular, we consider simple series-parallel circuits, series-parallel circuits and general circuits.

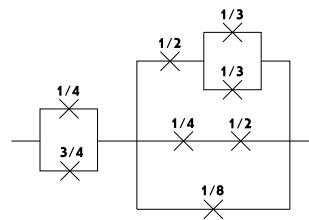
- (a) In class we discussed an algorithm (called the B-algorithm) for synthesizing simple series-parallel circuits for realizing probabilities of the form $a/2^n$, where $0 \leq a \leq 2^n$. Use the B-algorithm to synthesize a simple series-parallel circuit that computes $115/512$ using only $1/2$ -pswitches; draw the circuit. Draw a circuit that computes $397/512$ using $1/2$ -pswitches. How are the two circuits you synthesized related? Show your work.
- (b) What is the probability that the following series-parallel circuit is closed? Show your work. Can you increase the probability that the following circuit is closed by exchanging the probabilities of two pswitches? Show your work.



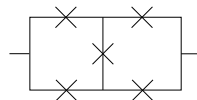- (c) What is the probability that the following non-series-parallel circuits are closed? Assume that each pswitch is closed with probability $1/2$. Show your work.
- i.



ii.

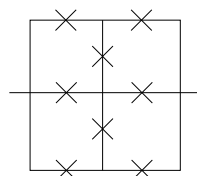

2. Linear Threshold (LT) Gates (*Collaboration is allowed on this Problem*)

A linear threshold gate computes a Boolean function $f(X)$ as follows,

$$f(X) = \text{sgn}(F(X)) = \text{sgn}\left(w_0 + \sum_{i=1}^n w_i x_i\right)$$

where,

$$\text{sgn}(F(X)) = \begin{cases} 0 & \text{if } F(X) < 0 \\ 1 & \text{if } F(X) \geq 0 \end{cases}$$

We say that a Boolean function is in the class LT_1 if it can be computed by a single LT gate. An LT circuit is a circuit that consists of LT gates.

- (a) Recall (from HW#4) that the Complete Quadratic (CQ) function is the Boolean function that consists of the XOR of all the $\binom{n}{2}$ possible AND 's between pairs of inputs. Namely,

$$CQ(X) = (x_1 \cdot x_2) \oplus (x_1 \cdot x_3) \oplus \cdots \oplus (x_{n-1} \cdot x_n)$$

Draw a depth-2 *layered* LT circuit that computes $CQ(X)$ with six inputs, namely, $X \in \{0, 1\}^6$. Please use as few LT gates as possible. We expect you to use the method (due to Muroga) that was described in class.

- (b) We generalize linear threshold functions to accept more than two possible values in their inputs. Assume that every input x_i to a threshold function comes from an alphabet of size q , namely, $x_i \in \{0, 1, 2, \dots, q-1\}$ (the binary case is when $q = 2$, namely, $x_i \in \{0, 1\}$). For this generalization, we define the functions OR_q and AND_q as follows:

$$OR_q(x_1, x_2, \dots, x_n) = \begin{cases} 0 & \text{if } x_i = 0 \text{ for all } 1 \leq i \leq n \\ 1 & \text{otherwise} \end{cases}$$

and

$$AND_q(x_1, x_2, \dots, x_n) = \begin{cases} 1 & \text{if } x_i \neq 0 \text{ for all } 1 \leq i \leq n \\ 0 & \text{otherwise} \end{cases}$$

- i. For which $q \geq 2$ is $OR_q \in LT_1$? Prove your claim.
- ii. For which $q \geq 2$ is $AND_q \in LT_1$? Prove your claim.